

ECE 253 Lecture Notes

Hei Shing Cheung

Digital and Computer Systems, Fall 2025

ECE253

The up-to-date version of this document can be found at <https://github.com/HaysonC/skulenotes>

Chapter 1

Digital Circuits that Compute, Store, and Control

Introduction

Layers of Computation In hardware, we have the following layers of abstraction:

- Computation
- Adders
- Logic Gates
- Transistors
- Silicon

In this course, we will focus on the first three layers, on top of the logic gate level.

Layer of abstraction At this course, for the digital systems part, we would start from understanding logic gates, all the way to understanding computer architecture, with each level of abstraction hiding the details of the lower level.

1.0.1 Hierarchy, Modularity, and Regularity

Definiton 1.0.1.1 (Hierarchy). The division of system into a set of modules, then further subdividing each module into smaller modules, and so on, until pieces are *easy* to understand.

Definiton 1.0.1.2 (Modularity). The design principle that modules have well-defined functions and interfaces so they connect easily without unintended side effects.

Definiton 1.0.1.3 (Regularity). The uniformity of modules, such that the reusability of common modules reduces the number of distinct modules to be designed.

1.0.2 Digital Logic Gates

Logic gates are made out of transistors:

Definiton 1.0.2.1 (Transistor). A transistor is a 3-terminal device behaving as a switch. When the voltage on the terminal is HI, the switch is closed, and when the voltage is LO, the switch is open.

Factors Affecting Speed of Digital Circuits

- **Transistors and Electrons take time to switch.** A transistor (State of the Art) takes 2-3 picoseconds to switch. Gates takes 40 ps and an 8-bit adder takes 300 ps.
- **Wires take time to propagate signals.** Signals travel at approximately 2/3 the speed of light in a vacuum, which is about 200,000 kilometers per second in a typical silicon wire.
- **Capacitance** There would be RCL circuits formed by the wires and transistors, which would cause delay.

1.1 Information Representation

1.1.1 Number Systems

Definiton 1.1.1.1 (Number System). A number system is a way of representing numbers using a set of symbols (digits) and a base (radix). The base determines the number of unique digits that can be used in the number system.

Common Number Systems You should be familiar with the following number systems:

1.1. INFORMATION REPRESENTATION

- Decimal (Base 10): Digits 0-9
- Binary (Base 2): Digits 0-1
- Hexadecimal (Base 16): Digits 0-9, A-F

In computer systems, we use binary to represent information, and we would often use hexadecimal to represent binary numbers in a more compact way - a group of 4 bits (a nibble) can be represented by a single hexadecimal digit.

Example 1.1.1.2 (Binary, Decimal, and Hexadecimal Numbers). Below is a table showing the conversion of binary numbers to decimal numbers, along with their hexadecimal representation.

Binary	Decimal	Hexadecimal
0000	0	0
0001	1	1
0010	2	2
0011	3	3
0100	4	4
0101	5	5
0110	6	6
0111	7	7
1000	8	8
1001	9	9
1010	10	A
1011	11	B
1100	12	C
1101	13	D
1110	14	E
1111	15	F

Table 1.1: Binary to Decimal and Hexadecimal Conversion

Example 1.1.1.3 (Decimal to Binary Conversion). To convert a decimal number to binary, we can use the method of successive division by 2. For example, to convert the decimal number 437 to binary:

$437 \div 2 = 218$	remainder 1
$218 \div 2 = 109$	remainder 0
$109 \div 2 = 54$	remainder 1
$54 \div 2 = 27$	remainder 0
$27 \div 2 = 13$	remainder 1
$13 \div 2 = 6$	remainder 1
$6 \div 2 = 3$	remainder 0
$3 \div 2 = 1$	remainder 1
$1 \div 2 = 0$	remainder 1

Reading the remainders from bottom to top, we get the binary representation of 437

1.1. INFORMATION REPRESENTATION

Example 1.1.1.4. To convert $(512000)_{10}$ to binary, we recognize that $512000 = 2^9 \times 1000$. We know that $2^9 = 512$ and $1000_{10} = 1111101000_2$ (by method outlined above). Therefore, we can shift the binary representation of 1000 left by 9 bits to get the binary representation of 512000:

$$(512000)_{10} = (11111010000000000000)_2$$

Note An alternative method is to divide by powers of 2.

Fractional Numbers. To represent fractional numbers in binary, we can use the method of successive multiplication by 2 (fixed point representation). Or we can use floating point representation, which is similar to scientific notation in decimal.

1.1.2 Binary Arithmetic and Logic

Binary Arithmetic Binary arithmetic is similar to decimal arithmetic, but it only uses two digits (0 and 1). Addition is associated with a sum and carry.

Binary Addition The rules for binary addition are as follows:

A	B	Sum, Carry
0	0	0, 0
0	1	1, 0
1	0	1, 0
1	1	0, 1

Table 1.2: Binary Addition

This could be summarized as the following logic:

$$\text{Sum} = A \oplus B, \quad \text{Carry} = A \cdot B \quad (1.1)$$

Binary Subtraction The rules for binary subtraction are defined using the addition of negative numbers (2's complement):

Definition 1.1.2.1 (Least Significant Bit (LSB) and Most Significant Bit (MSB)). The least significant bit (LSB) is the rightmost bit in a binary number, while the most significant bit (MSB) is the leftmost bit.

Definition 1.1.2.2 (2's Complement). The 2's complement of a binary number is obtained by inverting all the bits (1's complement) and adding 1 to the least significant bit (LSB).

Example 1.1.2.3 (Number Inversion). To find the 2's complement of the binary number $(10110010)_2$:

1. Invert all the bits: $(01001101)_2$
2. Add 1 to the LSB:

$$\begin{array}{r} 01001101 \\ + 00000001 \\ \hline 01001110 \end{array}$$

Therefore, the 2's complement of $(10110010)_2$ is $(01001110)_2$.

1.2 Logic Circuits

Definiton 1.2.0.1 (Logic Function). A logic function $L : \{0, 1\}^n \rightarrow \{0, 1\}$ is a mathematical function that takes n binary inputs and produces a single binary output based on a set of rules.

Definiton 1.2.0.2 (Truth Table). A truth table is a tabular representation of a logic function that lists all possible combinations of input values and their corresponding output values.

Definiton 1.2.0.3 (Boolean Algebra). Boolean algebra is a branch of algebra that deals with binary variables and logical operations. It provides a set of rules and properties for manipulating and simplifying logic functions. The specific rules and properties would be covered in later lectures.

1.2.1 Transistors as Switches

Definiton 1.2.1.1 (Transistor). Transistor operates as a switch. The switch is open only when the gate is high. We denote the state of the gate as $x \in \{0, 1\}$, where 0 is LO and 1 is HI. If input end of the switch is HI, the output end could be modeled by the logic function:

$$L(x) = x$$

Example 1.2.1.2 (Serial Transistors). Consider two transistors connected in series, with the input end of the first transistor connected to HI. The output end of the second transistor can be modeled by the following truth table:

x_1	x_2	$L(x_1, x_2)$
0	0	0
0	1	0
1	0	0
1	1	1

Table 1.3: Truth Table for Two Transistors in Series

The logic function can be expressed as:

$$L(x_1, x_2) = x_1 \cdot x_2$$

where \cdot denotes the AND operation.

x_1	x_2	$L(x_1, x_2)$
0	0	0
0	1	1
1	0	1
1	1	1

Table 1.4: Truth Table for Two Transistors in Parallel

Example 1.2.1.3 (Parallel Transistors). Consider two transistors connected in parallel, with the input end of both transistors connected to HI. The output end can be modeled by the following truth table:

The logic function can be expressed as:

$$L(x_1, x_2) = x_1 + x_2$$

where $+$ denotes the OR operation.

Example 1.2.1.4. Consider a circuit with a transistor connected to LO and the output end connected to LO. The other ends of the output and the transistor are connected together to a HI (and a resistor). The output end of the circuit can be modeled by the following truth table:

x	$L(x)$
0	1
1	0

Table 1.5: Truth Table for a Transistor Connected to LO

The logic function can be expressed as:

$$L(x) = \bar{x}$$

where \bar{x} denotes the NOT operation.

1.2.2 Basic Logic Gates


Definiton 1.2.2.1 (AND Gate). An AND gate outputs 1 only if all inputs are 1. The truth table for a 2-input AND gate is shown in Table 1.3.

The logic function for an AND gate with inputs A and B can be expressed as:

$$L(A, B) = A \cdot B = AB$$

Note when no operator is present, it is assumed to be AND.

 The digital logic symbol for an AND gate is shown below:




1.2. LOGIC CIRCUITS

Definiton 1.2.2.2 (OR Gate). An OR gate outputs 1 if at least one input is 1. The truth table for a 2-input OR gate is shown in Table 1.4.

The logic function for an OR gate with inputs A and B can be expressed as:

$$L(A, B) = A + B$$

The digital logic symbol for an OR gate is shown below:

 


Definiton 1.2.2.3 (NOT Gate). A NOT gate outputs the inverse of the input. The truth table for a NOT gate is shown in Table 1.5.

The logic function for a NOT gate with input A can be expressed as:

$$L(A) = \overline{A}$$

 The digital logic symbol for a NOT gate is shown below:



1.2.3 Additional Logic Gates

Example 1.2.3.1 (XOR Operation). We have two switches, when both switches are in the same state (both open or both closed), the output is 0. When the switches are in different states (one open and one closed), the output is 1. The truth table for this operation is shown below:

x_1	x_2	$L(x_1, x_2)$
0	0	0
0	1	1
1	0	1
1	1	0

Table 1.6: Truth Table for XOR Operation

The logic function can be expressed as:

$$L(x_1, x_2) = x_1 \oplus x_2 = \overline{x_1}x_2 + x_1\overline{x_2}$$


where \oplus denotes the XOR operation.

Definiton 1.2.3.2 (XOR Gate). An XOR gate outputs 1 if the inputs are different. The truth table for a 2-input XOR gate is shown in Table 1.6.

The logic function for an XOR gate with inputs A and B can be expressed as:

$$L(A, B) = A \oplus B = \overline{A}B + A\overline{B}$$

 where \oplus denotes the XOR operation. The digital logic symbol for an XOR gate is shown below:




In addition, we have the following gates:

Definiton 1.2.3.3 (NAND Gate). A NAND gate outputs 0 only if all inputs are 1. The truth table for a 2-input NAND gate is shown in Table ??.

The logic function for a NAND gate with inputs A and B can be expressed as:

$$L(A, B) = \overline{A \cdot B} = \overline{A} + \overline{B}$$

The digital logic symbol for a NAND gate is shown below:

 

Definiton 1.2.3.4.

NAND and NOR Gates are Cheaper NAND gates and NOR gates are cheaper than AND and OR gates because they require fewer transistors to implement. A 2-input NAND gate can be implemented using 4 transistors, while a 2-input AND gate requires 6 transistors (4 for the NAND gate and 2 for the NOT gate). The same applies to NOR and OR gates.

NAND and NOR Gates are Universal (Functionally Complete) Additionally, NAND and NOR gates are universal gates, meaning that any logic function can be implemented using only NAND or NOR gates.

This makes them more versatile and cost-effective for building complex digital circuits.

Commonly Used Logic Operators Below is a table summarizing the commonly used logic operators:

Operator	Symbol	Description
AND	\cdot or no symbol	Outputs 1 if all inputs are 1
OR	$+$	Outputs 1 if at least one input is 1
NOT	\bar{x}	Outputs the inverse of the input
inverse	$'$ or \sim	Outputs the 2's complement of the input
XOR	\oplus	Outputs 1 if inputs are different
NAND	$\bar{\cdot}$	Outputs 0 if all inputs are 1
NOR	$\overline{+}$	Outputs 0 if at least one input is 1
XNOR	$\overline{\oplus}$	Outputs 1 if inputs are the same

Table 1.7: Commonly Used Logic Operators

1.3 Digital Storage Elements

1.4 Finite State Machines (FSM)

Chapter 2

Computer Organization and Assembly Language

What is Assembly Language? We know that we can run C/C++ on any computer (Machine Agnostic), but how does the computer understand C/C++? The answer is the compiler that parse it to assembly through:

1. **Front-end Parser:** The front-end parser would parse the C/C++ code into an intermediate representation (IR), which is a low-level representation of the code that is easier to optimize. The front-end parser would also perform optimizations on the IR, such as loop unrolling, inlining, and dead code elimination.
2. **Back-end Parser:** The back-end parser would take the optimized IR and generate assembly code for a specific architectures.

2.1. COMPUTER ORGANIZATION

The assembly code is then assembled into machine code, which is a series of 0s and 1s that the computer can understand. The assembly would be specific to the architecture of the computer (machine dependent), which is why we have different assembly languages for different architectures (e.g., x86, RISC-V, ARM).

2.1 Computer Organization

2.2 Assembly Language